

Reflex Lab 01 Reference Schematic

This is a reference connection schematic for the breadboard build. It is not a PCB layout.

Power

```
ESP32 3V3  -> breadboard + rail  
ESP32 GND  -> breadboard - rail
```

All signal returns share ESP32 GND.

Potentiometer Input

```
10 kOhm potentiometer outer leg -> 3V3  
10 kOhm potentiometer outer leg -> GND  
10 kOhm potentiometer wiper      -> GPIO34
```

GPIO34 is input-only on the ESP32, which makes it a good analog input for this course.

LED Output

```
GPIO25 -> 330 ohm resistor -> LED anode (+)  
LED cathode (-) -> GND
```

The resistor must stay in series with the LED.

Buzzer Output

```
GPIO26 -> 1 kOhm resistor -> passive piezo +  
passive piezo - -> GND
```

The dashboard records the guarded buzzer command as part of the evidence trace.

Button Input

```
GPIO27 -> tactile button -> GND
```

The firmware uses `INPUT_PULLUP`, so the button reads released when open and pressed when it connects GPIO27 to GND.

Signal Story

```
Pot(GPI034) -> threshold_reflex_v0 -> Guard -> LED(GPI025)
                                     Guard -> Buzzer(GPI026)
Button(GPI027) -----> Buzzer mute state
```

Future PCB Note

KiCad files are not required for the ESP32-001 breadboard release. If this course later grows a soldered or PCB variant, add KiCad source and PDF exports under this folder without changing the breadboard evidence claim.